

Lighten Up

You have two switches (**A** and **B**) and two lights (**L1** and **L2**). Both switches are initially off (and both lights are off).


What happens when you:

Turn on switch **A**?

Turn on switch **B**?

Turn on both **A** and **B** at the same time?

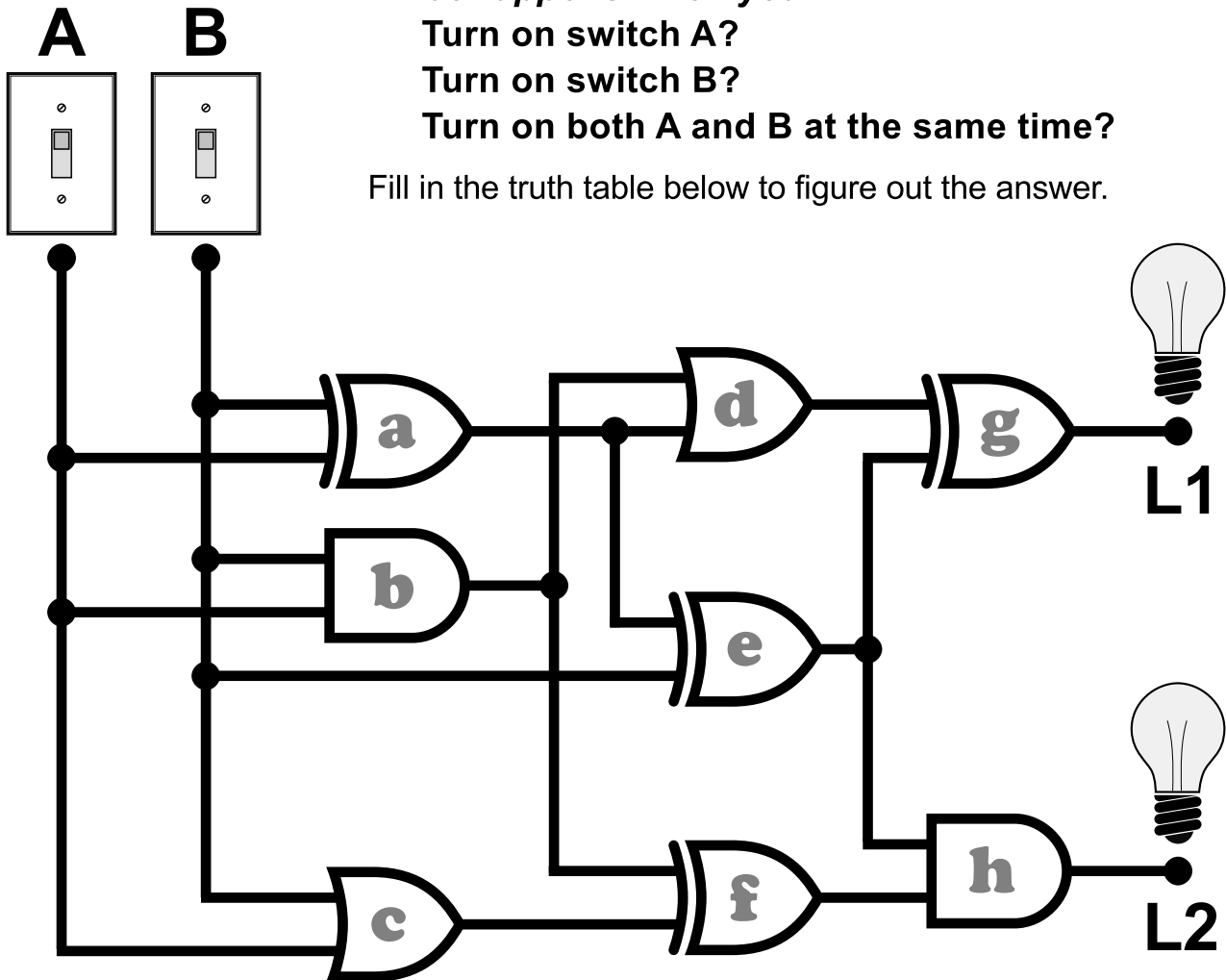Fill in the truth table below to figure out the answer.



| | <i>Switches</i> | | <i>Logic gates</i> | | | | | | | <i>Lights</i> | | | |
|----------------|-----------------|----------|--------------------|----------|----------|----------|----------|----------|----------|---------------|-----------|-----------|---------------------------------------|
| | A | B | a | b | c | d | e | f | g | h | L1 | L2 | |
| Both A & B off | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | Both lights off |
| Only B on | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | B turns on L1 |
| Only A on | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | A turns on L2 |
| Both A & B on | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | Both switches on = both lights off |