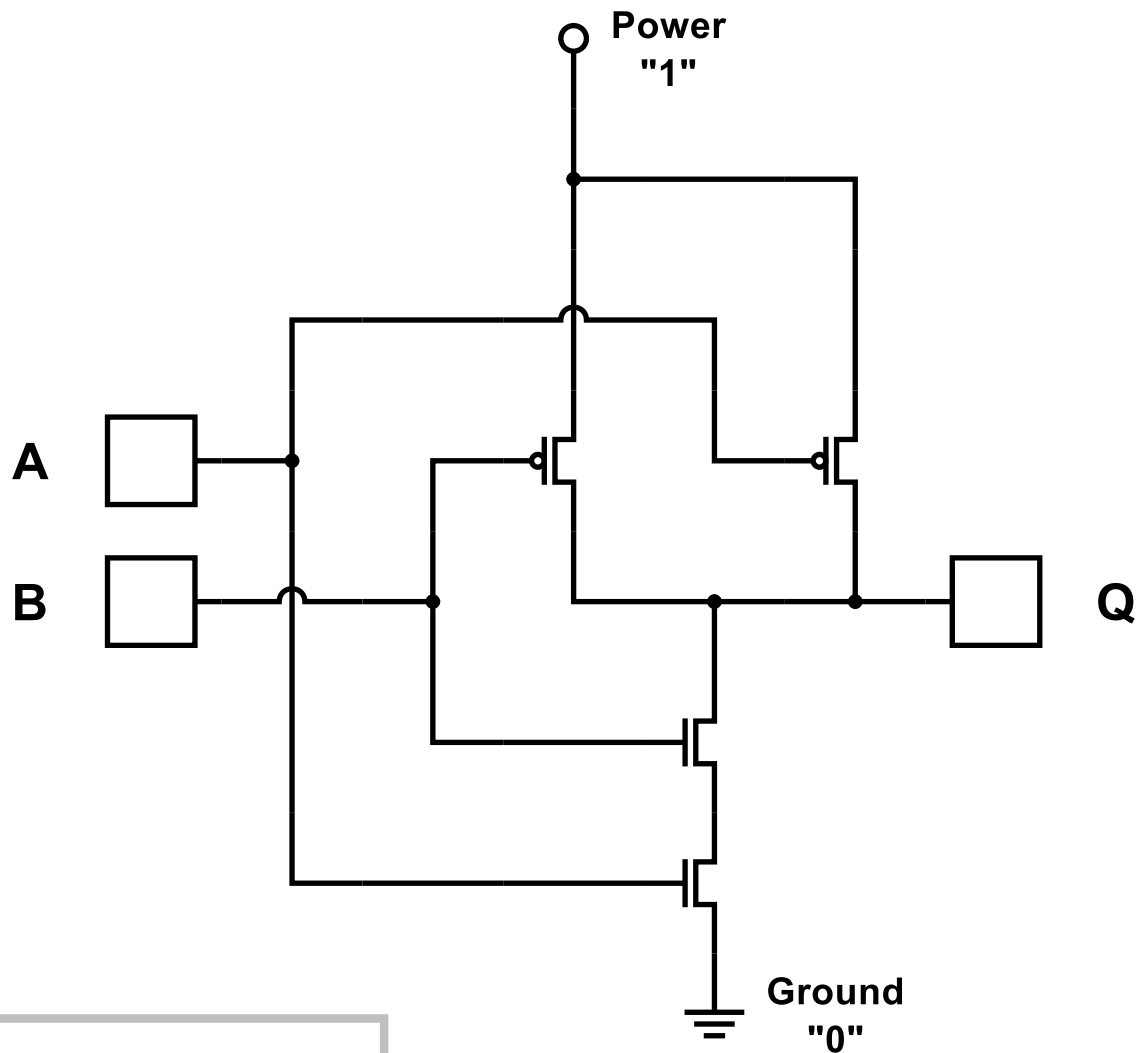


# CMOS #2

Plug in all the combinations of '0' and '1' values for A and B into this circuit and then follow the flow of electricity to determine Q for each pair of input values.

Fill in the Truth Table with your answers.



<b>A</b>	<b>B</b>	<b>Q</b>
<b>0</b>	<b>0</b>	_____
<b>0</b>	<b>1</b>	_____
<b>1</b>	<b>0</b>	_____
<b>1</b>	<b>1</b>	_____

Which logical operation does this implement?