
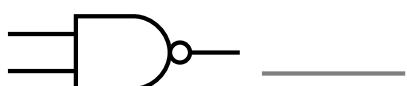
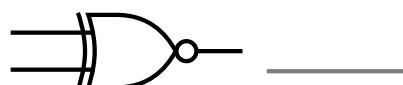
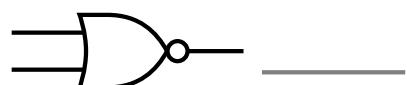
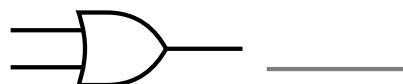
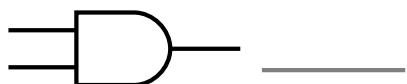
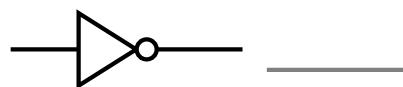


Name _____

Date _____

Logic Gate Symbols

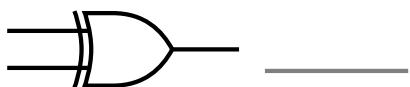Write the name of the logic operation (NOT, AND, OR, XOR, NAND, NOR, XNOR) that corresponds to each of the following logic gate symbols:



Write the name of the logic operation (NOT, AND, OR, XOR, NAND, NOR, XNOR) that corresponds to each of the following truth tables:

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

$$Q = A \underline{\hspace{1cm}} B$$

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

$$Q = A \underline{\hspace{1cm}} B$$

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

$$Q = A \underline{\hspace{1cm}} B$$

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

$$Q = A \underline{\hspace{1cm}} B$$

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

$$Q = A \underline{\hspace{1cm}} B$$

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

$$Q = A \underline{\hspace{1cm}} B$$

A	Q
0	1
1	0

$$Q = \underline{\hspace{1cm}} A$$